 


Computer Architecture Homework 4

Spring 2019, March


1 Synchronous Finite State Digital Machine Systems

- a. The circuit shown below can be simplified. Write a Boolean expression that represents the function of the simplified circuit using the minimum number of AND, OR, and NOT gate.




$$\overline{\overline{A}(B + \overline{C})} = A + \overline{(B + \overline{C})}$$
$$= A + \overline{B}C$$


Simplified Circuit:

 

 b. Consider the finite state machine below which has 6 states and a single input that can take on the value of 0 and 1. The finite state machine should output 1 IF AND ONLY IF 6 + sum of all the input values is not divisible by 2 or 3. One transition has been provided; complete the remainder of the diagram. (Hint: If the sum of the inputs is a multiple of 6, then we have 6 + sum of the inputs = 6n for some n. As 6n is divisible by 2, 6n cannot be prime.)



 c. Consider the following circuit. Assume registers have a CLK to Q time of 60ps, a setup time of 40ps, and a hold time of 30ps. Assuming that all gates have the same propagation delay, what is the maximum propagation delay each individual gate could have to achieve a clock rate of 1 GHz.



Suppose the maximum propagation delay is t_{pd}

The register delay is $\text{Setup} + \text{hold} = 0.1 \times 10^{-9} \text{ s}$

$$f(\text{register delay} + 3t_{pd}) = 1 \times 10^9$$

$$0.1 \times 10^{-9} + 3t_{pd} = 1 \times 10^{-9}$$

$$\Rightarrow t_{pd} = 0.3 \times 10^{-9} \text{ s} = 300 \text{ ps}$$

2 Boolean Logic

1. Simplify each Boolean expression to one of the following ten expressions:

$0, 1, A, B, AB, A + B, \overline{A} \overline{B}, \overline{A} + \overline{B}, A\overline{B}, \overline{A}B$

Each answer may be used as many times as necessary.

a. $A(A + \overline{A}) + B$

$$= AA + A\overline{A} + B = A + 0 + B = A + B$$

b. $(A + B)(\overline{A} + B)\overline{B}$

$$= [(A+B)\overline{A} + (A+B)B]\overline{B} = [B\overline{A} + AB + B]\overline{B} = [B\overline{A} + (A+1)B]\overline{B}$$

$$= [B(\overline{A}+1)]\overline{B} = 0$$

c. $\overline{\overline{A} + \overline{B}}$

$$= (\overline{\overline{A}})(\overline{\overline{B}}) = AB$$

2. Simplify the following expression step by step (as simple as possible):

a. Standard: $(A + B)(A + \overline{B})C$

$$= (A\overline{A} + A\overline{B} + BA)C = (A + A(\overline{B} + B))C = (A + A)C = AC$$

b. Grouping & Extra Terms: $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + ABC + A\overline{B}C$

$$= (\overline{A} + A)\overline{B}\overline{C} + (\overline{A}B + AB)\overline{C} + (A\overline{B} + A\overline{B})C$$

$$= \overline{B}\overline{C} + B\overline{C} + AC = \overline{C} + AC = \overline{C} + A$$

c. DeMorgan's: $\overline{A(\overline{B}\overline{C} + BC)}$

$$= \overline{A} + \overline{(\overline{B}\overline{C} + BC)} = \overline{A} + (\overline{\overline{B}\overline{C}})(\overline{BC})$$


$$= \overline{A} + (B+C)(\overline{B} + \overline{C}) = \overline{A} + B\overline{B} + B\overline{C} + C\overline{B} + C\overline{C} = \overline{A} + B\overline{C} + C\overline{B}$$

3 Logic Gates


- a. Create a NOT gate using only NAND gates.



 - b. Create an AND gate using only NAND gates. (Hint: use a)



 - c. Create an OR gate using only NAND gates.



- d. Create a NOR gate using only NAND gates. (Hint: use a & c)

